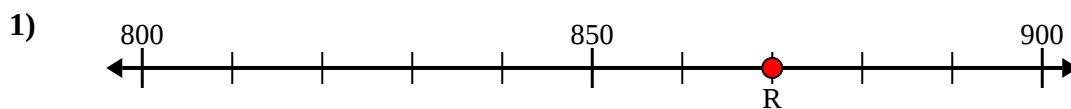





Find the value of R.

Answers


1. _____




2. _____

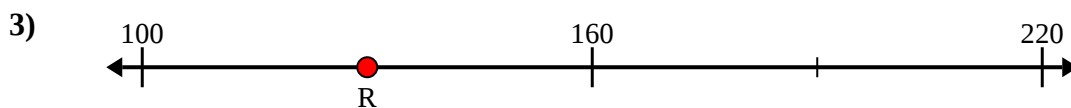


3. _____

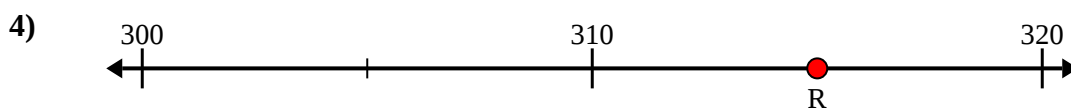


4. _____

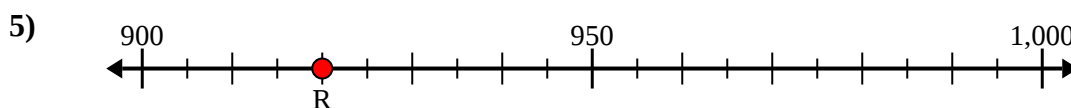


5. _____

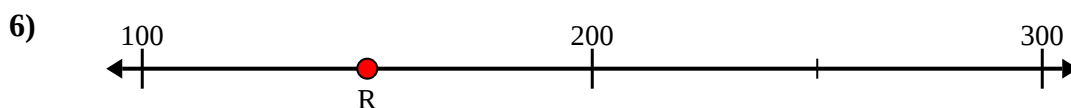


6. _____

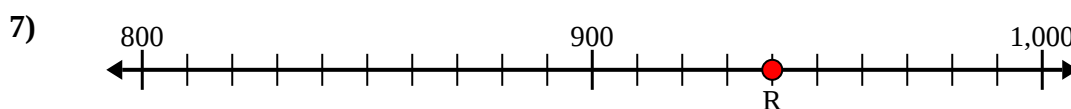


7. _____

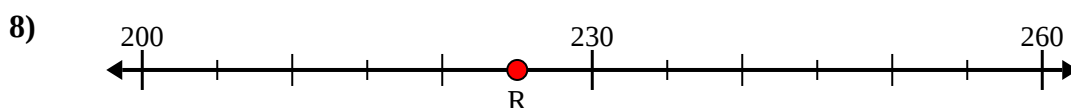

8. _____

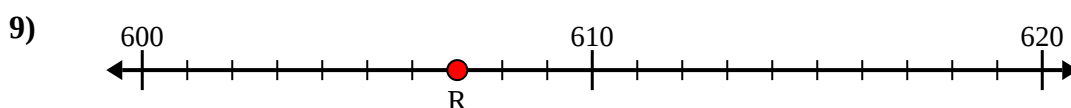











9. _____

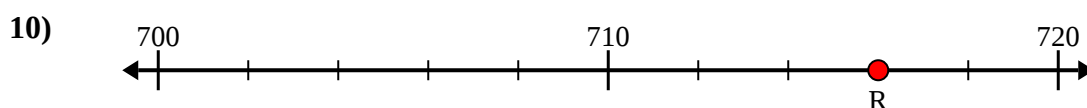

10. _____



Find the value of R.

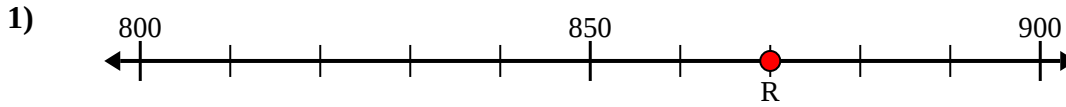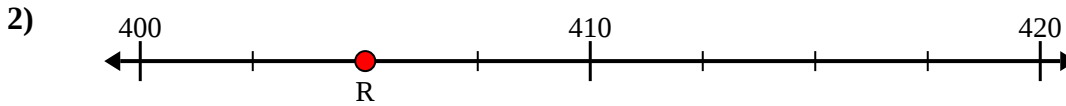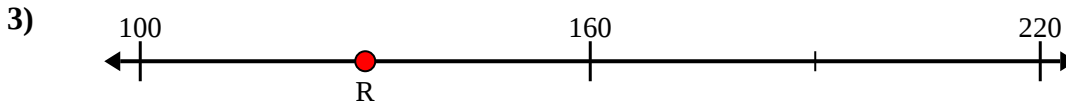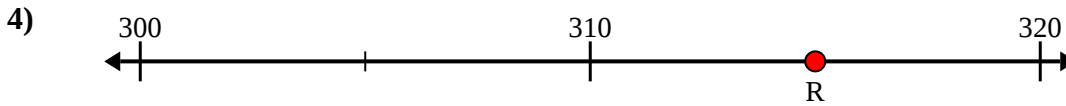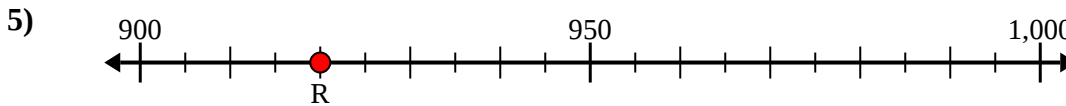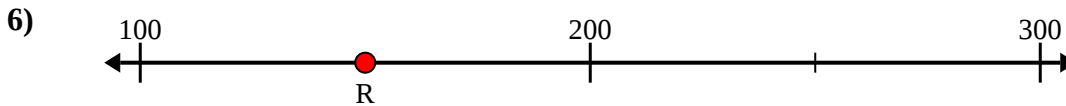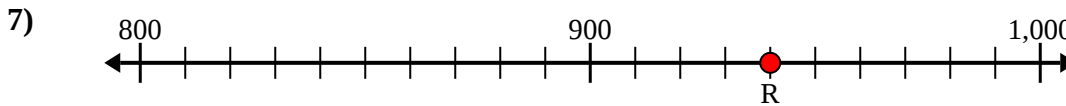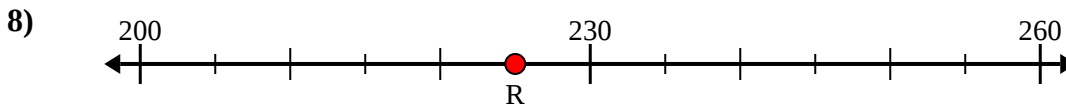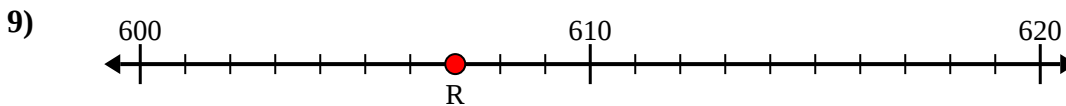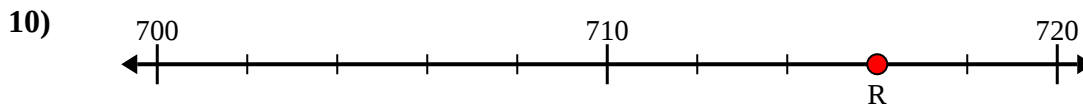Answers1. **870**2. **405**3. **130**4. **315**5. **920**6. **150**7. **940**8. **225**9. **607**10. **716**