
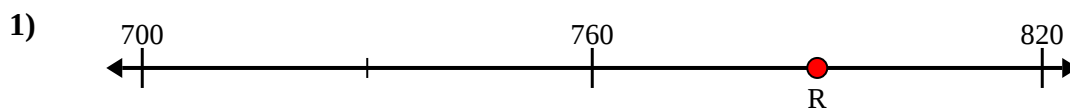


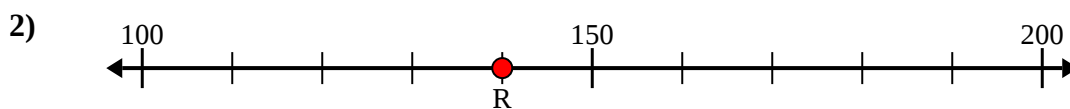


Find the value of R.

Answers


1. _____




2. _____

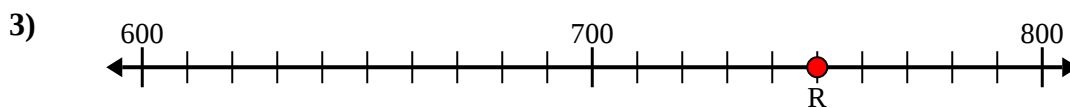


3. _____

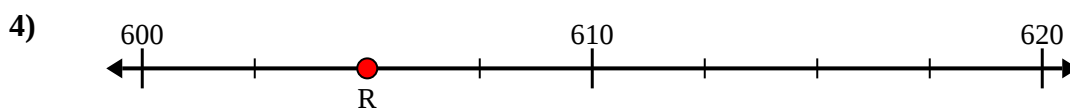


4. _____

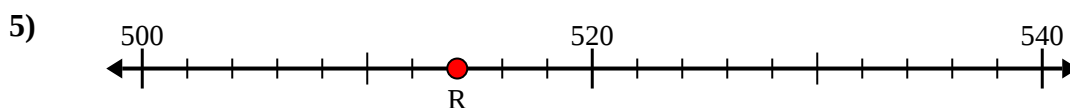


5. _____

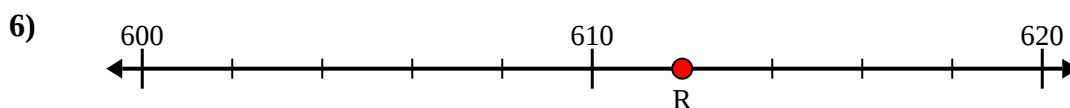


6. _____

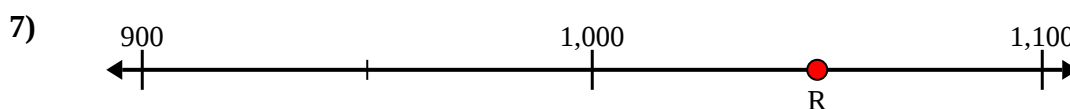


7. _____

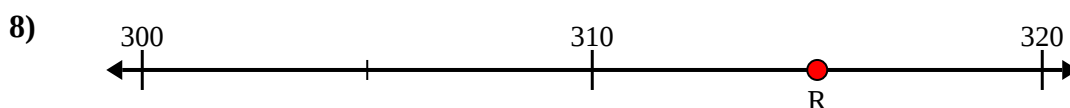

8. _____

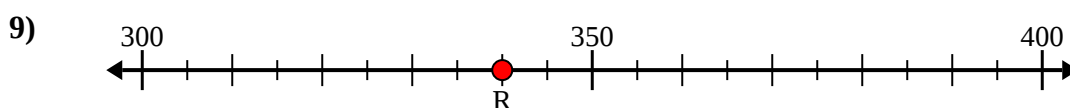











9. _____

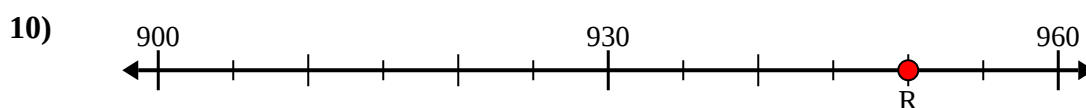

10. _____



Find the value of R.

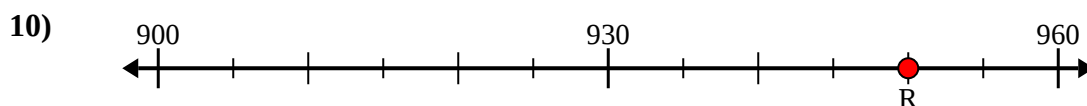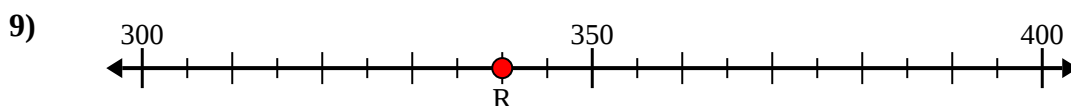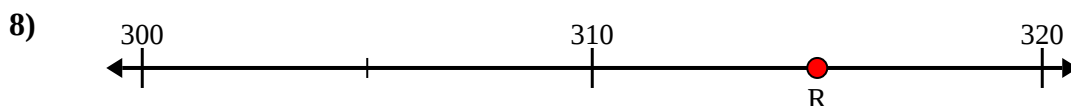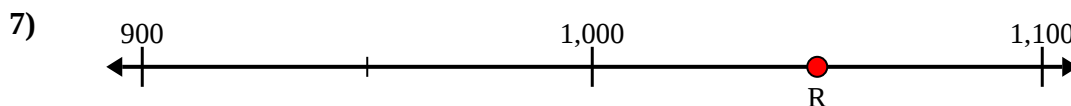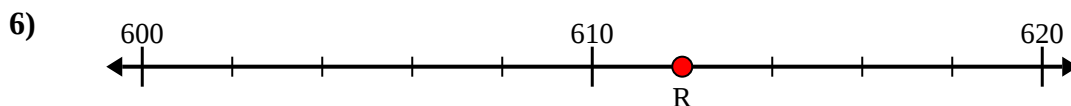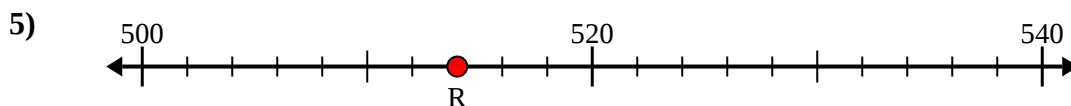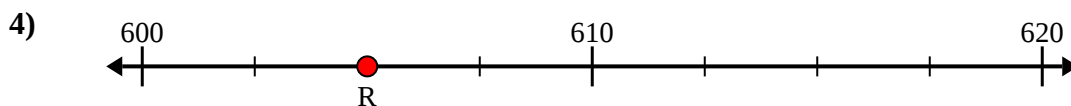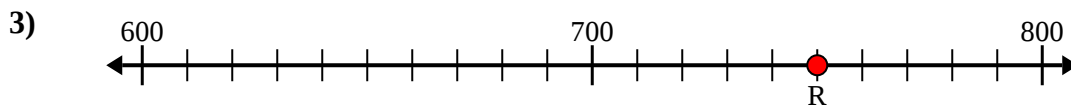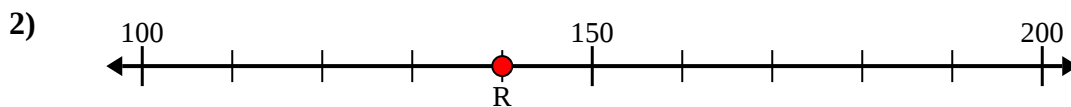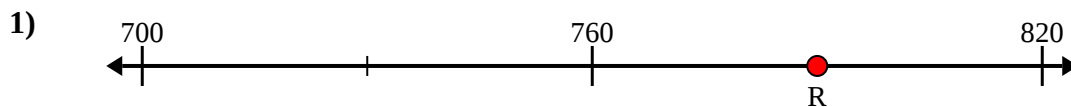**Answers**1. **790**2. **140**3. **750**4. **605**5. **514**6. **612**7. **1,050**8. **315**9. **340**10. **950**